

**The design project contains a set of specifications:**

- Power supply: +15V relative to the ground;
- Total quiescent current drawn from the power supply: no larger than 8 mA;
- No-load voltage gain (at 1 kHz):  $|A_{vo}| = 50 (\pm 10\%)$ ;
- Maximum no-load output voltage swing (at 1 kHz): no smaller than 8 V peak to peak;
- Loaded voltage gain (at 1 kHz and with  $R_L = 1\text{ k}\Omega$ ): no smaller than 90% of the no-load voltage gain;
- Maximum loaded output voltage swing (at 1 kHz and  $R_L = 1\text{ k}\Omega$ ): no smaller than 4 V peak to peak;
- Input resistance (at 1 kHz): no smaller than 50 k $\Omega$ ;
- Amplifier type: inverting or non-inverting;
- Frequency response: 20 Hz to 50 kHz (–3dB response);
- Type of transistors: BJT;
- Number of transistors (stages): no more than 3;
- Resistances permitted: values smaller than 220 k $\Omega$  from the E24 series;
- Capacitors permitted: 0.1  $\mu\text{F}$ , 1.0  $\mu\text{F}$ , 2.2  $\mu\text{F}$ , 4.7  $\mu\text{F}$ , 10  $\mu\text{F}$ , 47  $\mu\text{F}$ , 100  $\mu\text{F}$ , 220  $\mu\text{F}$ ;
- Other components (BJTs, diodes, Zener diodes, etc.): only from your ELE404 lab kit.

**Other specifications:**

- The output voltage must be free from distortions (clipping, etc.) in all test conditions. The source resistance,  $R_s$ , must be 600  $\Omega$  for all tests.
- The designed amplifier must be AC-coupled for the load and the signal source, but the coupling between its intermediate stages may be of AC or DC type as per the designer's choice.
- There are no restrictions in terms of using NPN or PNP transistors.